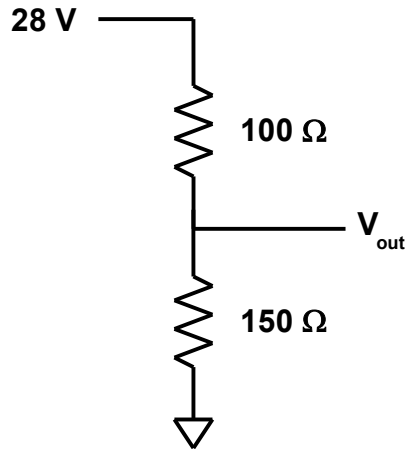



Final Exam – DC Circuits

1. The voltage drop across a 100 ohm resistor is $V = 0.2\text{V}$. The current through the resistor is _____.
 - a. 0.025 A
 - b. 0.003 A
 - c. 0.002 A
 - d. 0.004 A
2. The current through a 5 k Ω resistor is 0.1 mA. The voltage drop across the resistor is _____.
 - a. 4 V
 - b. 0.1 V
 - c. 3 V
 - d. 0.5 V
3. The voltage drop across a resistor is 0.5 V. The current through the resistor is 0.2 mA. The resistance of the resistor is _____.
 - a. 2500 Ω
 - b. 250 Ω
 - c. 1470 Ω
 - d. 3000 Ω
4. A 100 Ω resistor has a current of 40 mA running through it. The power dissipated through the resistor is _____.
 - a. 0.08 W
 - b. 0.16 W
 - c. 1 W
 - d. 0.32 W
5. The resistor in the problem above is used in a circuit with the same power dissipation. A minimal acceptable power rating for this resistor is _____.
 - a. 0.1 W
 - b. 0.08 W
 - c. 0.2 W
 - d. 0.05 W
6. Three resistors are connected in series having values of 150 Ω , 200 Ω , and 350 Ω . The total resistance is _____.
 - a. 700 Ω
 - b. 350 Ω
 - c. 200 Ω
 - d. 70 Ω

7. Two resistors are connected in parallel having values of $4.7 \text{ k}\Omega$ and $10 \text{ k}\Omega$. The total resistance is _____.
- $1.47 \text{ k}\Omega$
 - $5.17 \text{ k}\Omega$
 - $4.70 \text{ k}\Omega$
 - $3.20 \text{ k}\Omega$



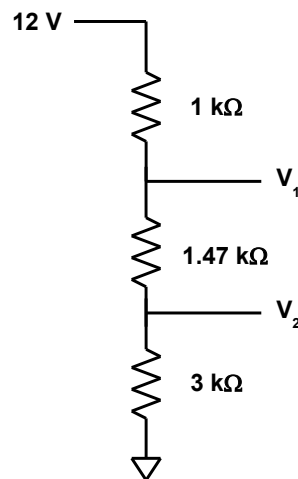8. The output voltage of the voltage divider shown above is _____.
- 20.4 V
 - 16.8 V
 - 28.0 V
 - 12.1 V




9. The output voltage, V_1 , of the voltage divider shown above is _____.
- 9.81 V
 - 8.87 V
 - 10.3 V

d. 7.46 V

10. The output voltage, V_2 , of the voltage divider in the previous problem is _____.

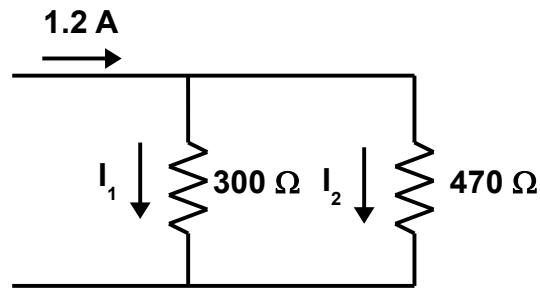- a. 5.13 V
- b. 7.24 V
- c. 5.73 V
- d. 6.58 V




11. The branch current, I_1 , in the current divider shown above is _____.

- a. 0.648 A
- b. 0.632 A
- c. 0.732 A
- d. 0.823 A

12. The branch current, I_2 , in the current divider in the previous problem is _____.

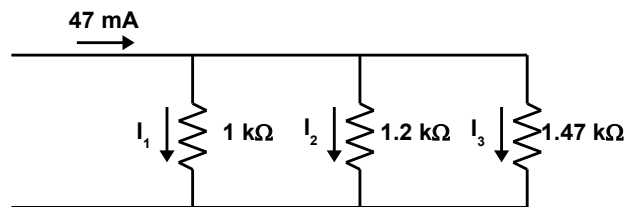- a. 0.672 A
- b. 0.468 A
- c. 0.734 A
- d. 0.832 A



13. The branch current, I_1 , in the current divider shown above is _____.

- a. 17.3 mA
- b. 16.8 mA
- c. 19.5 mA
- d. 18.7 mA

14. The branch current, I_2 , in the current divider in the previous problem is _____.

- a. 15.6 mA


- b. 17.8 mA
- c. 12.2 mA
- d. 9.87 mA

15. The branch current, I_3 , in the current divider in the previous problem is _____.

- a. 13.3 mA
- b. 15.2 mA
- c. 12.7 mA
- d. 21.3 mA

16. Voltage is added when flowing through a source, and subtracted when flowing through a resistor. Conventional current flow is defined as the same direction as _____ charges flow.

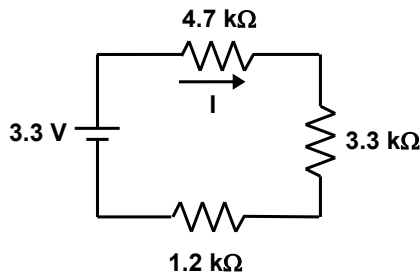- a. negative
- b. no
- c. positive
- d. all



17. For the series circuit shown above, the current I in the circuit is _____.

- a. 642 μA
- b. 267 μA
- c. 481 μA
- d. 359 μA

18. The voltage drop in the 4.7 k Ω resistor in the series circuit in the previous problem is _____.

- a. 2.73 V
- b. 1.12 V
- c. 3.72 V
- d. 1.69 V


19. The voltage drop in the 3.3 k Ω resistor in the series circuit in the previous problem is _____.

- a. 1.18 V
- b. 2.68 V

- c. 0.432 V
- d. 3.12 V

20. The voltage drop in the 1.2 kΩ resistor in the series circuit in the previous problem is _____.

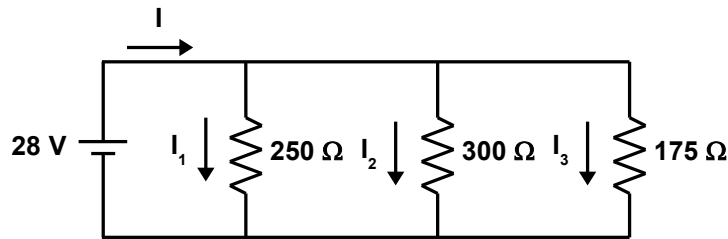- a. 0.213 V
- b. 0.430 V
- c. 1.75 V
- d. 0.127 V



21. For the parallel circuit shown above, the current I_1 is _____.

- a. 0.212 A
- b. 0.416 A
- c. 0.314 A
- d. 0.112 A

22. For the parallel circuit in the previous problem, the current I_2 is _____.

- a. 0.127 A
- b. 0.213 A
- c. 0.0933 A
- d. 0.372 A

23. For the parallel circuit in the previous problem, the current I_3 is _____.


- a. 0.160 A
- b. 0.153 A
- c. 0.172 A
- d. 0.281 A

24. For the parallel circuit in the previous problem, the total current I is _____.

- a. 0.214 A
- b. 0.576 A
- c. 0.365 A
- d. 0.127 A

25. For the parallel circuit in the previous problem, the voltage drop across the resistors is _____.

- a. 14 V
- b. 28 V
- c. 32 V
- d. 17 V

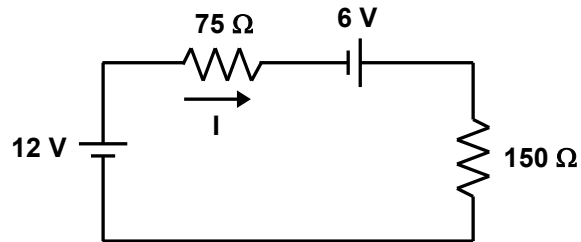

26. In the circuit shown above, the current I is _____.


- a. 0.12 A
- b. 0.05 A
- c. 0.17 A
- d. 0.08 A

27. In the circuit in the previous problem, the voltage drop in the $75\ \Omega$ resistor is _____.

- a. 6 V
- b. 8 V
- c. 10 V
- d. 12 V

28. In the circuit in the previous problem, the voltage drop in the $150\ \Omega$ resistor is _____.

- a. 6 V
- b. 8 V
- c. 12 V
- d. 10 V

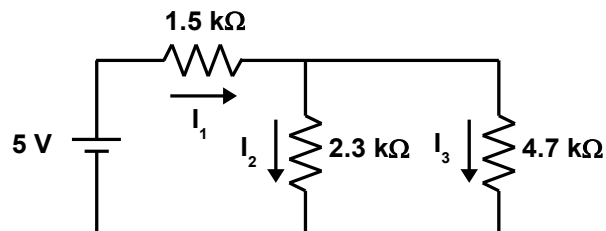

29. In the circuit shown above, the current I_1 is _____.

- a. 2.73 mA
- b. 3.67 mA


- c. 0.157 mA
- d. 1.64 mA

30. In the circuit in the previous problem, the current I_2 is _____.

- a. 2.35 mA
- b. 0.812 mA
- c. 3.72 mA
- d. 1.10 mA

31. In the circuit in the previous problem, the current I_3 is _____.

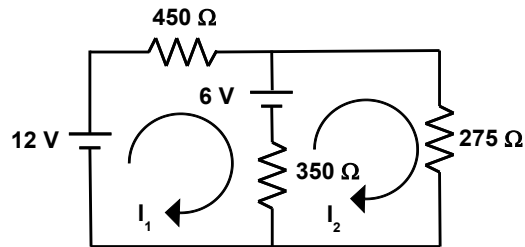- a. 0.214 mA
- b. 0.0126 mA
- c. 0.540 mA
- d. 0.725 mA




32. In the circuit shown above, the mesh current I_1 is _____.

- a. 0.0155 A
- b. 0.0286 A
- c. 0.127 A
- d. 0.00861 A

33. In the circuit in the previous problem, the mesh current I_2 is _____.

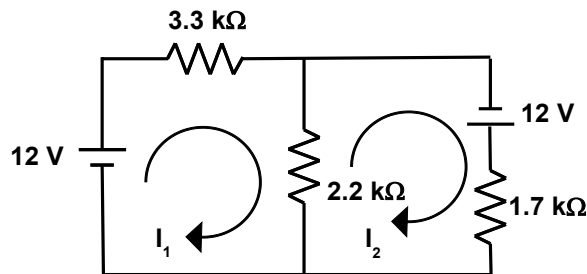- a. 0.0297 A
- b. 0.372 A
- c. 0.218 A
- d. 0.0183 A



34. In the circuit shown above, the mesh current I_1 is _____.

- a. 4.41 mA
 - b. 2.76 mA
 - c. 8.23 mA
 - d. 5.91 mA
35. In the circuit in the previous problem, the mesh current I_2 is _____.
- a. 8.71 mA
 - b. 1.23 mA
 - c. 5.56 mA
 - d. 2.42 mA
36. A series circuit has _____ path(s) for current flow.
- e. two
 - f. one
 - g. multiple
 - h. no
37. A parallel circuit has _____ path(s) for current flow.
- a. only one
 - b. only two
 - c. multiple
 - d. no
38. It is ok to dissipate 10 watts of power through a resistor that is rated for 2 watts.
- a. False
 - b. True
39. Power dissipation in a resistor _____ as resistance increases.
- a. increases
 - b. decreases
 - c. stays the same
 - d. none of the above
40. Voltage equals _____ times resistance.
- a. voltage
 - b. resistance
 - c. power
 - d. current
41. The equation in the above problem is known as _____ Law.
- a. Tesla's
 - b. Maxwell's
 - c. Ohm's

- d. Faraday's
42. An ohm is defined as the electrical resistance between two points of a conductor when a constant potential difference of _____, applied to these points, produces in the conductor a current of 1 amp.
- a. 0 volts
 - b. 1 volt
 - c. 1000 volts
 - d. 2 volts
43. In order to determine the current through a resistor, you must know the resistance as well as the _____ across the resistor.
- a. voltage
 - b. capacitance
 - c. inductance
 - d. magnetic field strength
44. Power is measured in _____.
- a. Watts
 - b. Ohms
 - c. Volts
 - d. Joules
45. In order to find the total resistance in a series circuit, you must _____ each resistor value.
- a. subtract
 - b. multiply
 - c. add
 - d. divide